

Homework Problem:

Design and implement (structural and behavioral) following mealy(overlap) sequence detector

Given input symbols is $\Sigma = \{a,b\}$
output symbols is $\Lambda = \{Y,N\}$

The FSM should outputs a Y at a time instance k only if the last 4 inputs were ***aabb or bbaa***.

Note: On reset input the state should be RST state and output is don't care.

Hints:

step1:Identify different states

step2:Draw state diagram

step3:Use binary encoding of states and write state table

step4:Obtain next state and output equations

step5:Implement Using D flip flops and logic gates (you can use any logic gates)

step6:Write VHDL code in structural

step7:Verify the FSM using simulation

step8 Verify the same using Virtual Jtag

step9: Implement the VHDL code in behavioral style (from the state diagram) and repeat steps 7 and 8 and Confirm the FSM inferred from the Quartus tool is correct

TRACEFILE format: reset input clock output mask