Virtual JTAG based Scan Chain to test Krypton CPLD

Abhinav Sridhar Wadhwani Electronics Lab IIT Bombay



Objectives

- Need for scan chain
- Basic understanding of JTAG and Scan Chain
- What is Virtual JTAG IP
- How to Run scan chain using virtual JTAG
- Some FAQs



Why Test on Hardware?

- Why to test on Hardware?
- We have written a testbench and thoroughly tested it with a tracefile
- Not just RTL but also Gate level simulations show zero errors in design
- Why do we need test our design on hardware again?



Why Test on Hardware?

- Why to test on Hardware?
- We have written a testbench and thoroughly tested it with a tracefile
- Not just RTL but also Gate level simulations show zero errors in design
- Why do we need test our design on hardware again?
- Gate Level files merely mimic the hardware
- Hardware may have some other timing differences, or a small fault in hardware
- The design may not be synthesizable (it still may work on software)
- All simulated designs may not work perfectly on board




Why Scan Chain?

- Designs tested so far using I/O pins:
 - o 1 bit full adder, 4:1 MUX, 3:8 Decoder
- Can we test 4 bit adder-subtractor on board?
 - Solution: Add 1 more switch
- How to test 4 bit 4:1 multiplexers?
 - Add 10 switches for the 18 inputs
- What about bigger designs like an 16 bit adders?
- How many peripherals to add?
- Also manually testing 1 input may take around 1 second
- For 4 but 4:1 MUX, 2¹⁸ sec => 72+ hours
- How to test designs?
- Solution: Scan Chain



JTAG

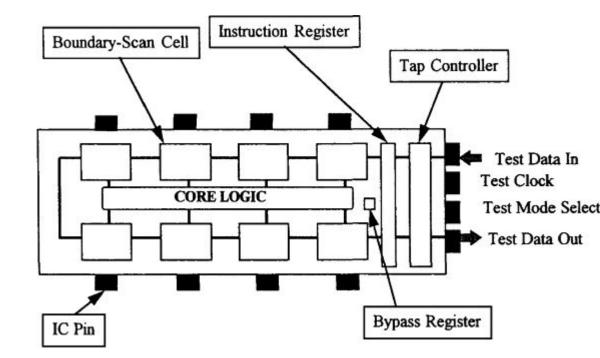- Joint Test Action Group
- Industry standard for verifying designs and testing PCBs
- Connects to an on-chip Test
 Access Port (TAP) controller
- TAP controller implements a protocol to access a set of registers or pins of a system
- Response is then stored into Flip-Flops and then compared with a golden response







JTAG

- The testing is controlled with the help of the following pins
 - o TDI
 - o TDO
 - TMS
 - o TCLK
 - TRST (optional)
- Normal operation: the test inputs are bypassed, circuit works as specified
- Testing mode: The boundary scan cells take the input set by the TAP controller, and output of each register or wire is stored in the flipflops

Normal operation

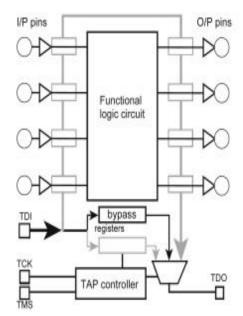

Testing

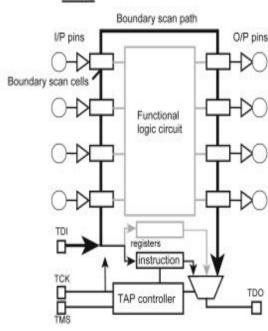





JTAG

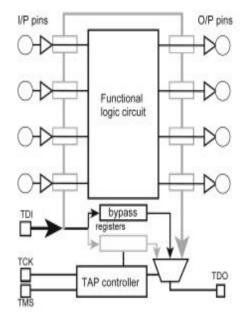- Used to compare it to golden response
- This is also called scan mode
- Flipflops connected in chained manner
 SCAN CHAIN
- TDI: Test Data IN
- TDO: Test Data OUT
- TCK: Test Clock
- TMS: Test Mode Select
- TRST: Test RESET (Optional as per the protocol)






Testing

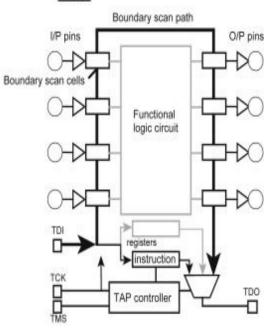



Virtual JTAG

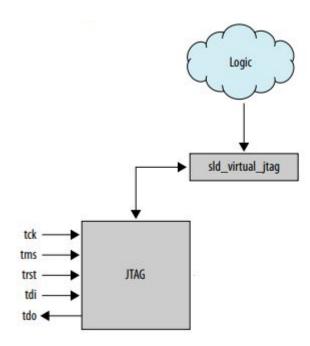
- Virtual JTAG Intel FPGA IP Core
- Intellectual Property: complete source code not visible
- Feature of the on-chip debugging tool suite
- The python commands (through the exe file) sends the JTAG commands through USB
- This IP core enables an easy way to customize a JTAG scan chain internal to the device via FTDI (USB)





Virtual JTAG

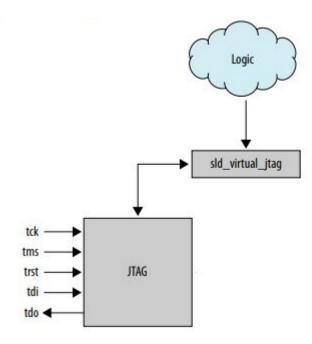- Objective of the course => Digital design using FPGA
- Virtual JTAG based scan chain to be viewed as blackbox
- For more details, visit the <u>Intel Virtual JTAG IP User Guide</u>
- Implementation details are out of the scope of this course





Steps to Run Virtual JTAG

Design: Vidur Shah, Gaurav Kate

Documentation: Soumyajit Langal, Abhinav Sridhar



Install Python, PIP, Python Packages

- Install Python 3.7 or Python 3.8
- Install PIP
- Install the following packages using the commands as shown
 - pip install bitstring
 - pip install ftd2xx
 - pip install pyusb



Setup Environment

- Necessary files
 - DUT wrapped design file and other dependent design files with working RTL and Gate level simulations
 - Tracefile


- Files Required for Scan Chain (Shared)
 - TopLevel.vhd
 - Folder v_jatg
 - scan_vjtag.exe file
 - scan_vjtag.py

Copy these files and paste them in the project directory



Modifications to Quartus Project

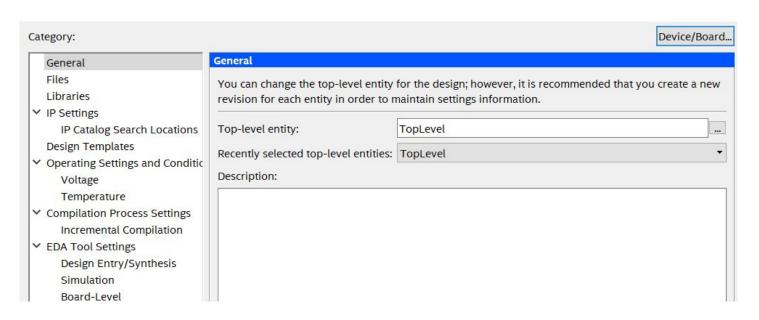
- Add TopLevel.vhdl to the Quartus Project
- Add the number of inputs and outputs to the design in lines 20 and 21 respectively
- This change is the same as what was done for testbench
- Go to Assignments -> Settings -> General
- Set top level entity as TopLevel as shown





Modifications to Quartus Project

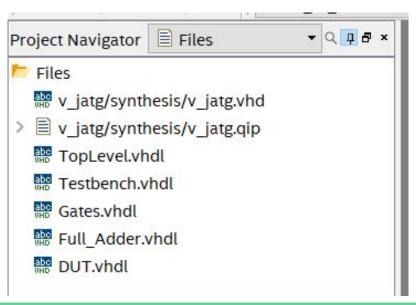- Add the following files in the path: v_jtag\synthesis
 - v_jatg.vhd
 - o v_jatg.qip
- For a sample full adder project, these are the list of files that have to be present
- Note that the presence or absence of testbench in the project does not matter during scan chain





Quartus Instructions

- Do a full compilation of the design (note you need to repeat the task since the top level entity has changed)
- Generate SVF file again
- Dump the SVF file on the Krypton Board
- TURN OFF THE KRYPTON BOARD AND TURN IT ON AGAIN USING THE POWER SWITCH GIVEN
- Open Command Prompt and change path



Change Path using CD command

- Open Command Prompt and change path using cd command
- In case the project is on C drive, use the following
 - o cd ..\..
 - o cd <absolute path from C drive>

```
C:\Users\abhin>cd ..\..
C:\>cd intelFPGA_lite\18.1\
```

- This path can be copied from windows explorer
- In case you are in D/E/F drives, enter the following
 - D: or E: or F:
 - cd <absolute path from D/E/F drive>

```
C:\Users\abhin>D:
D:\>cd IIT_Bombay\WEL\NPTEL\Scan_Chain_Test\Full_Adder_code_files
```



Run Scan Chain

- Run the following command to observe the output
 - scan_vjtag.exe TRACEFILE.txt out.txt

```
D:\IIT_Bombay\WEL\NPTEL\Scan_Chain_Test\Full_Adder_code_files>scan_vjtag.exe TRACEFILE.txt out.txt
{'type': 6, 'id': 67330064, 'description': b'Dual RS232-HS A', 'serial': b'A'}
```

- scan_vjtag.exe is the name of the file to run
- TRACEFILE.txt needs to be a text file in the specified format. It is an input to the exe file
- In case you have renamed it, write the new file name in the command
- out.txt is a file that is generated by the code. There need not be an existing file with the name.
 In case there is, the program will overwrite the file without warnings
- Check out.txt to find whether your design has successfully passed all test cases or not



Frequently Encountered Errors

- In case you get the below error, turn off the Krypton board and turn it on again
- Then repeat the last command: scan_vjtag.exe TRACEFILE.txt out.txt

```
D:\IIT_Bombay\WEL\NPTEL\Scan_Chain_Test\Full_Adder_code_files>scan_vjtag.exe TRACEFILE.txt out.txt
Traceback (most recent call last):
   File "scan_vjtag.py", line 11, in <module>
        dev = ftd.open(0)
   File "ftd2xx\ftd2xx.py", line 100, in open
   File "ftd2xx\ftd2xx.py", line 44, in call_ft
ftd2xx.ftd2xx.DeviceError: DEVICE_NOT_OPENED
[18740] Failed to execute script scan_vjtag
```



Frequently Encountered Errors

- In case the .exe file is treated as a virus by your antivirus software, then give it permission by allowing the file in settings
- If the issue still persists, the scan_vjtag.py file is provided as backup
- Verify installation of the pip packages in slide 12 (enter installation command again and you will get something similar to the following if it is installed successfully)

```
D:\IIT_Bombay\WEL\NPTEL\Scan_Chain_Test\Full_Adder_code_files>pip install pyusb
Requirement already satisfied: pyusb in c:\users\abhin\appdata\local\programs\python\python38-32\lib\site-packages (1.0.2)
```

- Repeat all steps until the command scan_vjtag.exe TRACEFILE.txt out.txt
- Enter the following command instead of that
 - python scan_vjtag.py TRACEFILE.txt out.txt

```
D:\IIT_Bombay\WEL\NPTEL\Scan_Chain_Test\Full_Adder_code_files>python scan_vjtag.py TRACEFILE.txt out.txt {'type': 6, 'id': 67330064, 'description': b'Dual RS232-HS A', 'serial': b'A'}
```



Frequently Encountered Errors

- In case Quartus throws an error unrelated to your design, then do the following
- Verify the port names in v_jtag.vhd with the component declared in TopLevel.vhd
- Before dumping the SVF file, open pin planner and map it as shown in image (also mentioned in comments of TopLevel.vhdl
- Compile design again, and proceed from slide 16

1	Named: * × «» Edit: ×		PIN_51	
	Node Name	Direction	Location	I/O Bank
0	state_out[4]	Output	PIN_58	4
c	state_out[3]	Output	PIN_57	4
9	state_out[2]	Output	PIN_55	4
0	state_out[1]	Output	PIN_53	4
0	state_out[0]	Output	PIN_51	4
	< <new node="">></new>	1 14.7		



THANK YOU

